

**Bilkent University**  
**Computer Science Department**  
**CS224 – COMPUTER ORGANIZATION**  
**Preliminary Design Report**  
**Lab 5**  
**Section 4**  
**Seçkin Alp Kargı**  
**22001942**  
**24/11/2023**

## B) List of Hazards

Name of Hazard	Type of Hazard	Affected Stages	Solutions
compute-use	Data hazard	Instruction Decode Execute (Memory and WriteBack when wrong values come)	Forwarding Stalling
load-use	Data Hazard	Instruction Decode Execute Memory	Stalling
load-store	Data Hazard	Memory Execute	Stalling
J-type jump	Control Hazard	Instruction Fetch Instruction Decode	Inserting Nop Stalling
branch	Control Hazard	Instruction Fetch Instruction Decode	Stalling 3 cycles, Branch Prediction

### Explanations, What, When, How:

#### Compute-use:

##### What is Compute-Use:

It is a particular form of data hazard that arises when a computation instruction relies on the outcome of a preceding instruction, and dependent instruction attempts to utilize the result before it has become accessible.

##### When it is Happening:

In R-type instructions for instance sub \$t1, \$t2, \$t3, add \$t2, \$t4, \$t1 in here before the changes done for \$t1 in sub instruction, add instruction tries to use \$t1.

##### How it is Happening:

For example, if we have two instructions that can cause compute use, first IF stage fetch than ID and RF starts at the same time second IF stage fetch. Then first execution starts for example sub instruction performs the subtraction, at the same time second IF and Rf stage happening. For add reads \$t4, and \$t1, in here we need \$t1 is value stored in previous sub instruction. In execution 2 add instruction tries the add the values \$t4 and \$t1 but register 4 sub \$t1, \$t2, \$t3, add \$t2, \$t4, \$t1 is not updated yet.

##### Possible Solutions:

**Forwarding:** If the result of the sub is available in the execute stage, it can be forwarded directly to the decode stage, allowing the add to use the most recent value. It increases the performance.

**Stalling:** The pipeline can insert a stall or bubble; it will delay the execution of the add until the sub instruction's result is available in the write back stage. It decreases the performance.

## **Load-use:**

### **What is Load-Use:**

It is a particular form of data hazard that arises when one instruction to load data is reliant on the outcome of an earlier instruction to load data, and the dependent instruction attempts to utilize the loaded data before it is ready.

### **When it is Happening:**

It happens after the using of lw (lw \$s0, 0(\$s1)) following instruction tries to use source register (sub \$s2, \$s0, \$s4).

### **How it is Happening:**

For example, if we have two instructions that can cause load use, second instruction need to access data from \$s0 that modifying in the first instruction for that first instruction needs to complete memory stage. But it did not so it happens in this situation. Second instruction unable to access.

### **Possible Solutions:**

**Stalling:** The pipeline can insert a stall or bubble, The dependent instruction is not executed until the data from the load instruction is accessible, due to the stall. The pipeline may wait for the necessary data during the stall as no new instructions are retrieved or executed during that time. It decreases the performance.

## **Load-store:**

### **What is Load-Store:**

It is a particular form of data hazard that arises when an instruction to load data attempts to use stored data before it has been written to memory because it depends on the outcome of an earlier operation to store data.

### **When it is Happening:**

It happens if we use sw and lw that has same rt immediately. -> sw \$s0, 0(\$s1), lw \$s0, 0(\$s2)

### **How it is Happening:**

Writing the data to memory upon encountering a store instruction takes time. A dependent load instruction may try to use the data before it has been stored, leading to an inaccurate computation, if it is scheduled to run before the store instruction has finished storing the data.

### **Possible Solutions:**

**Stalling:** The pipeline can insert a stall or bubble; it will delay the execution of the sw until the lw instruction's result is available in the write back stage. It decreases the performance.

## **Branch:**

### **What is Branch:**

It is control hazard that arises when the next instructions start before we finished the new branch address's location.

### **When it is Happening:**

If we use branch instruction it happens.

### **How it is Happening:**

For example, `beq $s0,$s2, Next`. Normally if we do not have branch, it will go simply next instruction but we have branch and we do not know where we go to before the second instruction's starting to fetch.

### **Possible Solutions:**

**Stalling:** The pipeline can insert a stall or bubble; we can do this for 3 cycles.

**Branch Predicting:** We can try to predict the branch. We can do this by using three instructions. If we branch instruction exists other instruction will be cancelled. We can do branch decision in earlier.

## **j-type jump:**

### **What is J-type Jump:**

In MIPS assembly, the J-type jump instruction is an unconditional jump that moves execution to a different memory address, allowing the program to alter its control flow. It causes an instantaneous leap to the designated target address and has no conditions or dependencies.

### **When it is Happening:**

When we use J type instruction for example `J Next`.

### **How it is Happening:**

Next pipeline starts when j instruction is not finished

### **Possible Solutions:**

**Inserting Nop:** It will fill the pipeline until we completed to jump instruction.

**Stalling:** The pipeline can insert a stall or bubble; it will delay the execution of the next instruction until the j instruction's result is available in the write back stage. It decreases the performance.

## C) Logic Equations

**Input Signals:** BranchD, RsD, RtD, RsE, RtE, WriteRegE4:0, MemtoRegE, RegWriteE, WriteRegM4:0, MemtoRegM, RegWriteM, WriteRegW4:0, RegWriteW

**BranchStall** = (MemtoRegM AND BranchD AND (WriteRegM == rtD OR WriteRegM == rsD) OR (BranchD AND (WriteRegE == rsD OR WriteRegE == rtD) AND RegWriteE)

**lwStall** = MemtoRegE AND ((rtD == rtE) OR (rtE == rsD))

### Stalling:

**StallF**: StallF = (branchstall OR lwstall)

**StallD**: StallD = (branchstall OR lwstall)

### Flushing:

**FlushE**: FlushE = (branchstall OR lwstall)

### Forwarding:

**ForwardAD**: ForwardAD = RegWriteM AND (rsD != 0) AND (rsD == WriteRegM)

**ForwardBD**: ForwardBD = RegWriteM AND (rtD != 0) AND (rtD == WriteRegM)

### ForwardAE:

If ( RegWriteM AND (rsE != 0) AND ( rsE == WriteRegW))

ForwardAE = 10

else if ( RegWriteW AND (rsE != 0) AND ( rsE == WriteRegW))

ForwardAE = 01

Else

ForwardAE = 00

### ForwardBE:

If ( RegWriteM AND (rtE != 0) AND ( rtE == WriteRegW))

ForwardBE = 10

else if ( RegWriteW AND (rtE != 0) AND ( rtE == WriteRegW))

ForwardBE = 01

Else

ForwardBE = 00

## D) Fulfilled Pipelined MIPS Processor (Red Color for changes)

module PipeFtoD -> no change!

module PipeWtoF -> no change!

module PipeDtoE(input logic RegWriteD,MemtoRegD,MemWriteD,ALUSrcD,RegDstD,BranchD,clk,FlushE,reset

input logic [2:0] ALUControlD,

input logic [4:0] RsD, RtD, RdE,

input logic [31:0] SignImmD, RD1, RD2,

output logic RegWriteE, MemtoRegE, MemWriteE, ALUSrcE, RegDstE,

output logic [2:0] ALUControlE,

output logic [4:0] RsE, RtE, RdE,

output logic [31:0] SignImmE, RD1out,RD2out );

endmodule

module PipeEtoM(input logic clk, MemWriteE, RegWriteE, MemtoRegE, reset,

input logic [4:0] WriteDataE,

input logic [31:0] ALUoute, WriteDataE,

output logic RegWriteM, MemtoRegM, MemWriteM,

output logic [4:0] WriteRegM

output logic [31:0] AluOutM, WriteDataM );

endmodule

module PipeMtoW(input logic clk, RegWriteM, MemtoRegM, reset

input logic [4:0] WriteRegM,

input logic [31:0] RD, ALUOutM,

output logic RegWriteW, MemtoRegW,

output logic [4:0] WriteRegW,

output logic [31:0] ReadDataW, ALUOutW );

endmodule

```

module datapath (input logic clk, reset, RegWriteW,
                input logic[2:0] ALUControlD,
                input logic BranchD,
                input logic [31:0] pcPlus4D,
                input logic [31:0] ResultW,
                input logic [4:0] rsD,rtD,rdD,
                input logic [15:0] immD,
                input logic [4:0] WriteRegW,
                output logic RegWriteE,MemToRegE,MemWriteE,
                output logic[31:0] ALUOutE, WriteDataE,
                output logic [4:0] WriteRegE,
                output logic [31:0] PC, PCF, PCBranchE,
                output logic pcSrcE);

    logic stallF, stallD, ForwardAD, ForwardBD, FlushE, ForwardAE, ForwardBE;// Wires for connecting Hazard Unit

    logic [31:0] PcBranchD, PcPlus4F, PcSrcA, PcSrcB, ALUOutM, WriteDataM, ReadDataW, ALUOutW, PcPlus4D,
    SignImmD, SignImmDShifted, ResultW, SignImmE, SrcAE, SrcBE, ReadData, RD1Out, RD2Out, mx2Out, mx3Out;

    logic [4:0] WriteRegW, WriteRegE, WriteRegM, rsE, rtE, rdE, rsD, rtD, rdD;

    logic[2:0] ALUControlE;

    logic MemWriteM, MemtoRegW, ALUSrcE, RegDstE, RegWriteW;

    mux2 #32 mx1(PCPlus4F,PCBranchD,PCSrcD,PC');

    PipeWtoF pipe1(PC',StallF,clk,PCF);

    adder add1(PCF, 32'b04,PCPlus4F);

    PipeFtoD pipe2(RD,PCPlus4F,StallD,clk,InstrD,PCPlus4D);

    Imem imem1(PCF,RD);

    signext sign1(InstrD[15:0], SignImmD);

    sl2 sl21(SignImmD, SignShiftedOut);

    regfile rf (clk, regwrite, instr[25:21], instr[20:16], writeregW,result, srca, writedata);

    adder add2(SignShifted, PCPlus4D, PCBranchD);

    mux2 #32 mx2(RD1,ALUOutM,mx2Out);

    mux2 #32 mx3(RD2,ALUOutM,mx3Out);

    equal equal1(mx2Out,mx3Out,EqualD);

    and2 and21(BranchD, EqualD, PCSrcD);

```

```

PipeDtoE pipe3(RegWriteD,MemtoRegD,MemWriteD, ALUSrcD, RegDstD, BranchD, clk, FlushE, reset,
ALUControlD, RsD, RtD, RdE, SignImmD, RD1, RD2, RegWriteE, MemtoRegE, MemWriteE, ALUSrcE, RegDstE,
ALUControlE, RsE, RtE, RdE, SignImme, RD1out,RD2out);

mux2 #4 mx4(RtE,RdE,WriteRegE);

mux4 #32 mx5(RD1out,ResultW,ALUOutM,32'b0,SrcAE);

mux4 #32 mx6(RD2out,ResultW,ALUOutM,32'b0,WriteDataE);

mux2 #32 mx7(WriteDataE,SignImme,SrcBE);

alu alu1(SrcAE, SrcBE,ALUControlE,ALUOutE);

PipeEtoM pipe4(clk, MemWriteE, RegWriteE, MemtoRegE, reset, WriteDataE, ALUOutE, WriteDataE, RegWriteM,
MemtoRegM, MemWriteM, WriteRegM,ALUOutM, WriteDataM );

PipeMtoW pipe5(clk, RegWriteM, MemtoRegM, reset, WriteRegM , ALUOutM, RegWriteW, MemtoRegW,
WriteRegW, ReadDataW, ALUOutW);

mux2 #32 mx7(ReadDataW, ALUOutW, MemtoRegW,ResultW);

HazardUnit hazardunit1(RegWriteW, WriteRegW, RegWriteM,MemtoRegM, WriteRegM, RegWriteE,
MemtoRegE, rsE, rtE, rsD,rtD, ForwardAE,ForwardBE, ,StallD,StallF);

```

Endmodule

```

module HazardUnit( input logic RegWriteW,
    input logic [4:0] WriteRegW,
    input logic RegWriteM,MemtoRegM,
    input logic [4:0] WriteRegM,
    input logic RegWriteE,MemtoRegE,
    input logic [4:0] rsE,rtE,
    input logic [4:0] rsD,rtD,
    output logic [2:0] ForwardAE,ForwardBE,
    output logic FlushE,StallD,StallF
);

    Logic branchStall,lwStall;

    always_comb begin
        BranchStall = (MemtoRegM & BranchD & (WriteRegM == rtD | WriteRegM == rsD) | (BranchD & (WriteRegE == rsD |
WriteRegE = rtD) & RegWriteE);

        lwStall = MemtoRegE & ((rtD == rtE) | (rtE == rsD));

        ForwardAD = RegWriteM & (rsD != 0) & (rsD == WriteRegM);

        ForwardBD = RegWriteM & (rtD != 0) & (rtD == WriteRegM);

        StallD <= lwstall | branchstall;
    end

```



```

StallF <= lwstall | branchstall;

FlushE <= lwstall | branchstall;

If ( RegWriteM & (rsE != 0) & ( rsE == WriteRegW)) begin
    ForwardAE = 2b'10; end
    else if ( RegWriteW & (rsE != 0) & ( rsE == WriteRegW)) begin
        ForwardAE =2b'01; end
    Else
        ForwardAE = 2b'00;
If ( RegWriteM & (rtE != 0) & ( rtE == WriteRegW)) begin
    ForwardBE = 2b'10; end
    else if ( RegWriteW & (rtE != 0) & ( rtE == WriteRegW)) begin
        ForwardBE = 2b'01; end
    Else
        ForwardBE = 2b'00;

End

If ( RegWriteM & (rdE != 0) & ( rdE == WriteRegW)) begin
    ForwardCE = 2b'10; end
    else if ( RegWriteW & (rdE != 0) & ( rdE == WriteRegW)) begin
        ForwardCE = 2b'01; end
    Else
        ForwardCE = 2b'00;

end

module mips (input logic    clk, reset,
    output logic[31:0] pc,
    input logic[31:0] instr,
    output logic    memwrite,
    output logic[31:0] aluout, resultW,
    output logic[31:0] instrOut,
    input logic[31:0] readdata);

logic    memtoreg, pcsrc, zero, alusrc, regdst, regwrite, jump;
logic [2:0] alucontrol;

```

```

assign instrOut = instr;

controller controller1(input logic[5:0] op, funct, memtoreg, memwrite, alusrc, regdst, regwrite, jump, alucontrol,
branch);

datapath datapath1(clk, reset, RegWriteW, ALUControlD, BranchD, pcPlus4D, ResultW, rsD,rtD,rdD, immD,
WriteRegW,,RegWriteE, MemToRegE,MemWriteE, ALUOutE, WriteDataE, WriteRegE, PC, PCF, PCBranchE, pcSrcE);
);

endmodule

module imem ( input logic [5:0] addr, output logic [31:0] instr);

            8'h00: instr = 32'h20100019;  -> addi $t4, $zero, 25

            8'h04: instr = 32'h 2015003C;  -> addi $t5, $zero, 60

            8'h08: instr = 32'h 018C8825;  -> or $s3, $t5, $

            8'h0c: instr = 32' 218FFFF8;  -> addi $t7, $t4, -24

            8'h10: instr = 32'h 01F78020;  -> add $s5, $t4, $t7

            8'h14: t4instr = 32'h 2016001E;  -> addi $t6, $zero, 30

            8'h18: instr = 32'h 01AE9024;  -> and $s4, $t5, $t6

            8'h1c: instr = 32'h 01D6202A;  -> slt $a0, $t4, $t6

            8'h20: instr = 32'h 01AD8822;  -> sub $a2, $s4, $ t5

            8'h24: instr = 32'h 02948820;  -> add $a1, $s3, $s4

            8'h28: instr = 32' AE8D0014;  -> sw $s4, 0x14($t5)

            8'h2c: instr = 32' 8C020020;  -> lw $v0, 0x20($zero)

            default: instr = {32{1'bx}};    // unknown address

        endcase

endmodule

```

```

endmodule

```

### New Modules:

```

module equal(

    input wire [3:0] a,

    input wire [3:0] b,

    output wire out

);

    assign out = (a == b);

endmodule

```

```
module and2(  
    input wire a,  
    input wire b,  
    output wire out  
);  
    assign out = a & b;  
endmodule  
  
module Mux4(  
    input wire [3:0] data,  
    input wire [1:0] select,  
    output wire out  
);  
    assign out = (select == 2'b00) ? data[0] :  
        (select == 2'b01) ? data[1] :  
        (select == 2'b10) ? data[2] :  
        (select == 2'b11) ? data[3] :  
        1'bz;  
Endmodule
```

**Other Modules Does Not Need Changes.**

## E) Test Programs

### Test Code of No Hazard:

```
8'h00: instr = 32'h20100019;  -> addi $t4, $zero, 25
8'h04: instr = 32'h 2015003C;  -> addi $t5, $zero, 60
8'h08: instr = 32'h 018C8825;  -> or $s3, $t5, $
8'h0c: instr = 32' 218FFFF8;  -> addi $t7, $t4, -24
8'h10: instr = 32'h 01F78020;  -> add $s5, $t4, $t7
8'h14: t4instr = 32'h 2016001E;  -> addi $t6, $zero, 30
8'h18: instr = 32'h 01AE9024;  -> and $s4, $t5, $t6
8'h1c: instr = 32'h 01D6202A;  -> slt $a0, $t4, $t6
8'h20: instr = 32'h 01AD8822;  -> sub $a2, $s4, $ t5
8'h24: instr = 32'h 02948820;  -> add $a1, $s3, $s4
8'h28: instr = 32' AE8D0014;  -> sw $s4, 0x14($t5)
8'h2c: instr = 32' 8C020020;  -> lw $v0, 0x20($zero)
```

### Test Code of Compute-Use Hazard:

```
8'h00: instr = 32' 200E0004;  -> addi $t6, $zero, 4
8'h04: instr = 32'h 200D000E;  -> addi $t5, $zero, 14
8'h08: instr = 32'h 01AE8825;  -> or $t6, $t5, $t6
8'h0c: instr = 32'h 200C000A;  -> addi $t4, $zero, 10
8'h10: instr = 32'h 0231902A;  -> slt $s6, $t6, $s1
8'h14: instr = 32'h 02109020;  -> add $s5, $t4, $s0
8'h18: instr = 32'h 01CD8824;  -> and $s4, $t6, $t5
8'h1c: instr = 32'h 02AE8822;  -> sub $s7, $s5, $s6
8'h20: instr = 32'h 02A5A020;  -> add $s5, $s5, $s5
8'h24: instr = 32'h AEAD0014;  -> sw $s7, 0x14($t5)
8'h28: instr = 32' 8C020020;  -> lw $v0, 0x20($zero)
```

### **Test Code of Load-Use Hazard:**

8'h00: instr = 32'h 200D0005; -> addi \$t5, \$zero, 5  
8'h04: instr = 32'h AC0E0050; -> sw \$t6, 0x50(\$zero)  
8'h08: instr = 32'h 8C0F0050; -> lw \$t7, 0x50(\$zero)  
8'h0c: instr = 32'h 21CF0004; -> addi \$t7, \$t6, 4  
8'h10: instr = 32'h 97080048; -> lw \$t8, 0x48(\$t8)  
8'h14: instr = 32'h 21AD0003; -> addi \$t8, \$t5, 3  
8'h18: instr = 32'h 01F82022; -> sub \$t7, \$t7, \$t8  
8'h1c: instr = 32'h AC0F0085; -> sw \$t7, 0x85(\$zero)  
8'h20: instr = 32'h 8C0D0085; -> lw \$t5, 0x85(\$zero)  
8'h24: instr = 32'h 8DCF007C; -> lw \$t6, 0x7c(\$t5)  
8'h28: instr = 32'h 01AE4820; -> add \$t6, \$t5, \$t6  
8'h2c: instr = 32'h 200C0003; -> add \$t4, \$zero, 3

### **Test Code of Branch Hazards:**

8'h00: instr = 32'h 200C000A; -> addi \$t4, \$zero, 10  
8'h04: instr = 32'h 200D0006; -> addi \$t5, \$zero, 6  
8'h08: instr = 32'h 018C4820; -> add \$t6, \$t5, \$t4  
8'h0c: instr = 32'h 198D0004; -> beq \$t4, \$t5, 4  
8'h10: instr = 32'h 018D4822; -> sub \$t4, \$t4, \$t5  
8'h14: instr = 32'h 19AC0004; -> beq \$t5, \$t4, 4  
8'h18: instr = 32'h 25ADFFFE; -> addi \$t5, \$t5, -2  
8'h1c: instr = 32'h AC0E0030; -> sw \$t6, 0x30(\$zero)  
8'h20: instr = 32'h 018C482A; -> slt \$t5, \$t5, \$t4  
8'h24: instr = 32'h 018C4825; -> or \$t4, \$t5, \$t4  
8'h28: instr = 32'h 15A00004; -> beq \$t5, \$zero, 4  
8'h2c: instr = 32'h 018C4824; -> and \$t4, \$t5, \$t4  
8'h30: instr = 32'h 8C0F0030; -> lw \$t7, 0x30(\$zero)  
8'h34: instr = 32'h 198CFFFE; -> beq \$t4, \$t4, -2